

ELEC4320 Midterm Examination Sample

Part I: Short Questions

1. Write down the result of B for each of the following Verilog codes after execution:

i) `A <= 7'b1001010; B <= & A;`

B = 1'b0 (unary bit wise and)

ii) `A <= 7'b1001010; B <= A << 3;`

B = 7'b1010000 (left shift A by 3 bits)

iii) `A <= 4'b1001; B <= {2{A}};`

B = 8'b10011001 (replicate A twice)

2. You are going to implement a system running at 200MHz using a FPGA device. What should be the clock period constraint?


PERIOD = 5ns

3. What are the advantages of FPGA compared to processor? What are the main steps needed for implementing a design in FPGA?

FPGA can provide higher performance and lower power consumption than processor. The main steps include programming, pre-simulation, synthesis, implementation and post-simulation.

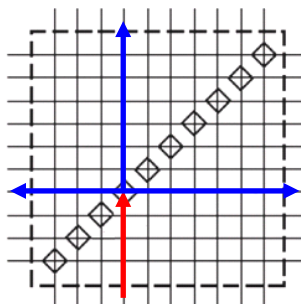4. For a switch block in FPGA, what is the meaning of flexibility? Given an example with figure.

Flexibility defines the number of other wire segments that each wire segment entering the switch block can be connected to.




```


module midtermQ1(
input clk,
output [7:0] result
);

reg[7:0] Z = 8'd0;
reg[7:0] A = 8'd1;
reg[7:0] B = 8'd2;
reg[7:0] C = 8'd3;

always@(posedge clk)
begin
    A <= B;
    B <= A + C;
    C <= B;
    Z <= A + B + C;
end

assign result = Z;
endmodule

```

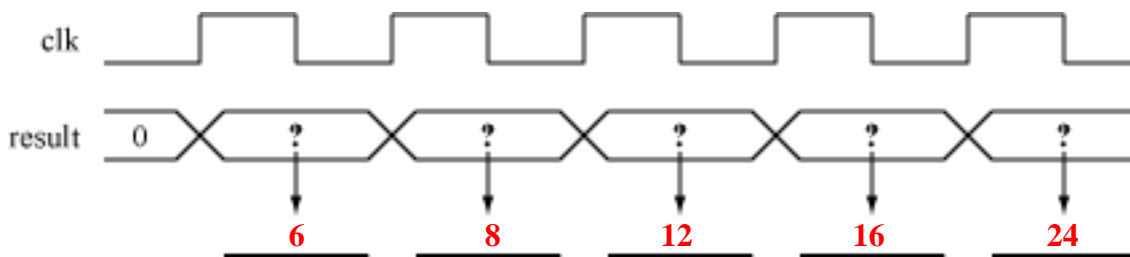

- b) Write up the Verilog code for implementing a 4-bit gray down counter by using two different modules: a 4-bit binary down counter module (**binCntD**) and a binary-to-gray module (**bin2gray**). Below shows the top module of the 4-bit gray down counter (**grayCntD**). Implement the three files: **grayCntD.v**, **binCntD.v** and **b2g.v**



grayCntD.v

```

module grayCntD
( input i_clk,
  input i_reset,
  output [3:0] o_gray_code
);

wire[3:0] bin_w;

binCntD binCntD
( .reset(i_reset),
  .clk(i_clk),
  .bin(bin_w)
);

b2g b2g
( .bin(bin_w),
  .gray(o_gray_code)
);

endmodule

```

b2g.v

```

module b2g
( input[3:0] bin,
  output[3:0] gray
);

assign gray = {bin[3], bin[3]^bin[2], bin[2]^bin[1], bin[1]^bin[0]};

endmodule

```

binCntD.v

```

module binCntD
( input reset,
  input clk,
  output reg[3:0] bin
);

reg[3:0] count = 4'd15;



always@(posedge clk)
begin
  if(reset)
  begin
    bin <= 4'b0;
  end
  else
  begin
    if( (count < 5'd16) || (count == 4'd0))
    begin
      bin <= count;
      count <= count -1;
    end
    else
      count <= 4'd15;
    end
  end
end

endmodule

```

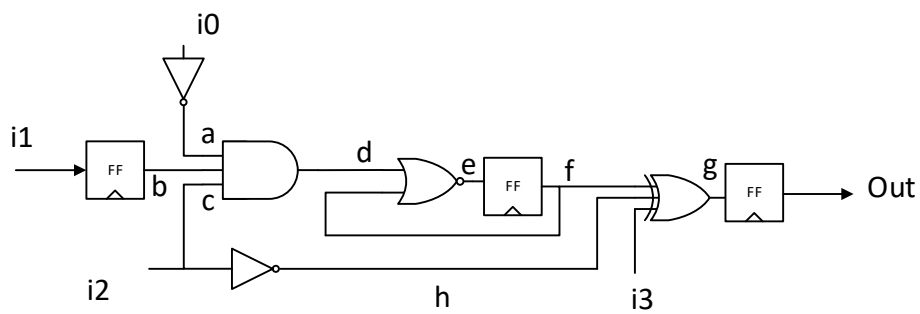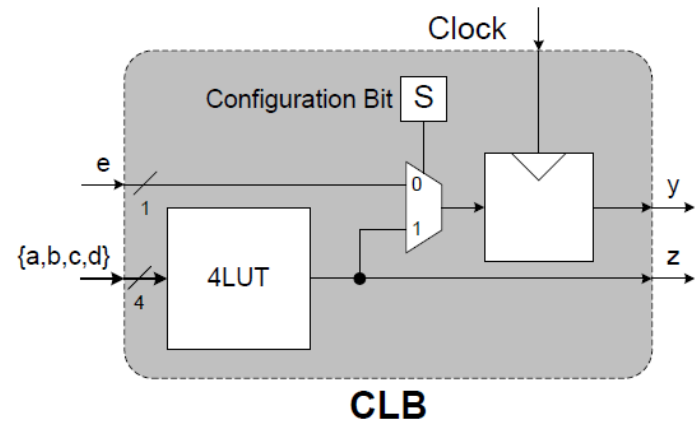2. Technology Mapping


Assuming a basic CLB as shown below, each CLB features a 4LUT, flip-flop and a mux to decide what input is connected to the flip-flop. Map the circuit shown directly below the CLB into as few of these CLBs as you can. You may connect each CLB input to a signal, logic 0, logic 1, or “nc” (for “no connection”). To answer the question, fill out the table at the bottom.



CLB inputs/outputs/configuration bits

	a	b	c	d	e	S	y	z
CLB1								
CLB2								
....								

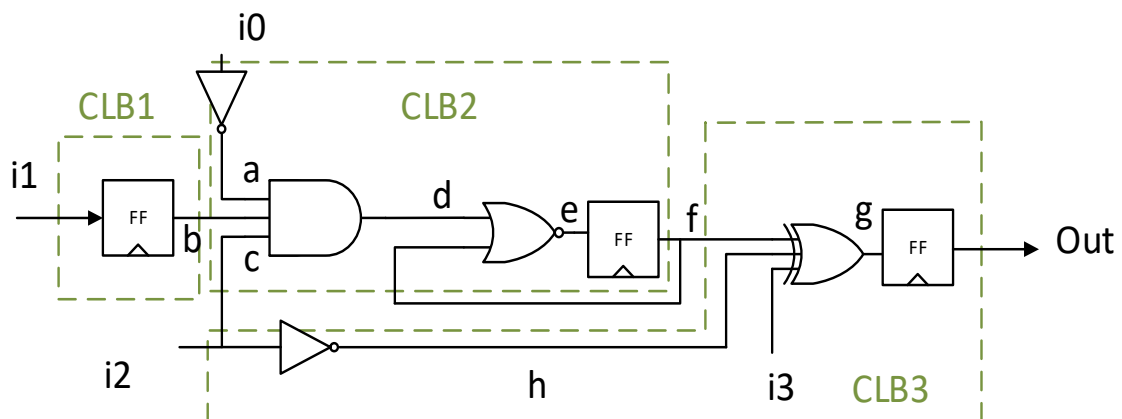Solution: The partition of the circuit is shown as follows.



The input/output of each CLB is shown in the table.

	a	b	c	d	e	S	y	z
CLB1					i1	0	b	
CLB2	i0	b	i2	f		1	f	
CLB3	f	i2	i3			1	Out	

3. High Level Synthesis

A function as shown in the code below is provided. It calculates the sum of first 'n' positive integers. Since 'n' is not known at compile time, none of the loop related optimizations can be applied. However, if we assuming that 'n' is always greater than 6, it is possible to apply at least one loop optimization.

- Can you suggest which optimization this might be?
- Can you rewrite the for-loop code in the optimized version?
- Can you suggest why the restructured for loop is better? Can you suggest any other optimization?

```
int running_sum(int n)
{
    int i;
    int sum = 0;
    for(i=1; i<=N; i++)
    {
        sum = sum + i;
    }
    return sum;
}
```

Fig. Given Code

- The loop optimization is “Loop Fission”

b)

```
int running_sum(int n)
{
    int i;
    int sum = 0;
    for(i=1; i<=6; i++)
    {
        sum = sum + i;
    }
}
```

c) The restructured for-loop as shown in b) is better because one can further unroll the first loop ($i = 1$ to 6) as a result of which its body can be executed in 1 clock cycle instead of 6 clock cycles. It is also possible to keep only the second loop ($i = 7$ to N) and initialize sum with the sum of first 6 integers (i.e. $1+2+3+4+5+6 = 21$) instead of zero.

END OF SAMPLE PAPER